

ELECTRICAL,
ELECTRONICS, AND
DIGITAL HARDWARE
ESSENTIALS FOR
SCIENTISTS AND
ENGINEERS

IEEE Press
445 Hoes Lane
Piscataway, NJ 08855

IEEE Press Editorial Board
John B. Anderson, *Editor in Chief*

R. Abhari
D. Goldof
M. Lanzerotti
T. Samad

G. W. Arnold
B-M. Haemmerli
O. P. Malik
G. Zobrist

F. Canavero
D. Jacobson
S. Nahavandi

Kenneth Moore, *Director of IEEE Book and Information Services (BIS)*

ELECTRICAL, ELECTRONICS, AND DIGITAL HARDWARE ESSENTIALS FOR SCIENTISTS AND ENGINEERS

Ed Lipiansky

Cisco Systems, Inc.
San Jose, California, USA



IEEE PRESS



IEEE PRESS SERIES ON MICROELECTRONIC SYSTEMS



A JOHN WILEY & SONS, INC., PUBLICATION

Cover Designer: Denise Lipiansky

Copyright © 2013 by The Institute of Electrical and Electronics Engineers, Inc.

Published by John Wiley & Sons, Inc., Hoboken, New Jersey. All rights reserved
Published simultaneously in Canada

No part of this publication may be reproduced, stored in a retrieval system, or transmitted in any form or by any means, electronic, mechanical, photocopying, recording, scanning, or otherwise, except as permitted under Section 107 or 108 of the 1976 United States Copyright Act, without either the prior written permission of the Publisher, or authorization through payment of the appropriate per-copy fee to the Copyright Clearance Center, Inc., 222 Rosewood Drive, Danvers, MA 01923, (978) 750-8400, fax (978) 750-4470, or on the web at www.copyright.com. Requests to the Publisher for permission should be addressed to the Permissions Department, John Wiley & Sons, Inc., 111 River Street, Hoboken, NJ 07030, (201) 748-6011, fax (201) 748-6008, or online at <http://www.wiley.com/go/permissions>.

Limit of Liability/Disclaimer of Warranty: While the publisher and author have used their best efforts in preparing this book, they make no representations or warranties with respect to the accuracy or completeness of the contents of this book and specifically disclaim any implied warranties of merchantability or fitness for a particular purpose. No warranty may be created or extended by sales representatives or written sales materials. The advice and strategies contained herein may not be suitable for your situation. You should consult with a professional where appropriate. Neither the publisher nor author shall be liable for any loss of profit or any other commercial damages, including but not limited to special, incidental, consequential, or other damages.

For general information on our other products and services or for technical support, please contact our Customer Care Department within the United States at (800) 762-2974, outside the United States at (317) 572-3993 or fax (317) 572-4002.

Wiley also publishes its books in a variety of electronic formats. Some content that appears in print may not be available in electronic formats. For more information about Wiley products, visit our web site at www.wiley.com.

Library of Congress Cataloging-in-Publication Data:

Lipiansky, Ed.

Electrical, electronics, and digital hardware essentials for scientists and engineers / Ed Lipiansky.

p. cm.

ISBN 978-1-118-30499-0 (hardback)

1. Electronic circuits. 2. Electronic apparatus and appliances. I. Title.

TK7876.L484 2012

621.3—dc23

2012012321

Printed in the United States of America

10 9 8 7 6 5 4 3 2 1

To my lovely wife Ruty

CONTENTS

Preface	xvii
About the Author	xix
1 From the Bottom Up: Voltages, Currents, and Electrical Components	1
1.1 An Introduction to Electric Charges and Atoms / 1	
1.2 Electric DC Voltage and Current Sources / 3	
1.2.1 Electric Current and Voltage / 3	
1.2.2 DC Voltage and Current Sources / 5	
1.2.3 Sources Internal Resistance / 9	
1.3 Electric Components: Resistors, Inductors, and Capacitors / 12	
1.3.1 Resistors / 12	
1.3.2 Resistors in Series and in Parallel / 19	
1.3.3 Resistivity: A Physical Interpretation / 23	
1.3.4 Resistance of Conductors / 25	
1.4 Ohm's Law, Power Delivered and Power Consumed / 25	
1.4.1 Voltage Source Internal Resistance / 30	
1.5 Capacitors / 33	
1.5.1 Physical Interpretation of a Parallel-Plate Capacitor Capacitance / 35	
1.5.2 Capacitor Voltage Current Relationship / 36	
1.5.3 Capacitors in Series / 37	
1.5.4 Capacitors in Parallel / 39	
1.5.5 Energy Stored in a Capacitor / 40	
1.5.6 Real Capacitor Parameters and Capacitor Types / 41	
1.6 Inductors / 44	
1.6.1 Magnetism / 45	
1.6.2 Magnetic Field around a Coil / 49	
1.6.3 Magnetic Materials and Permeability / 52	
1.6.4 Electromagnetic Induction and Inductor Current–Voltage Relationship / 53	

- 1.6.5 Inductors in Series / 58
- 1.6.6 Inductors in Parallel / 60
- 1.6.7 Mutual Inductance / 62
- 1.6.8 Energy Stored by an Inductor / 69
- 1.6.9 Inductor Nonlinearity / 70
- 1.6.10 Inductor Component Selection / 71
- 1.7 Kirchhoff's Voltage Law (KVL) and Kirchhoff's Current Law (KCL) / 73
- 1.8 Summary / 87
- Further Reading / 87
- Problems / 88

2 Alternating Current Circuits

98

- 2.1 AC Voltage and Current Sources, Root Mean Square Values (RMS), and Power / 98
 - 2.1.1 Ideal and Real AC Voltage Sources / 99
 - 2.1.2 Ideal and Real AC Current Sources / 106
- 2.2 Sinusoidal Steady State: Time and Frequency Domains / 111
 - 2.2.1 Resistor under Sinusoidal Steady State / 112
 - 2.2.2 Inductor under Sinusoidal Steady State / 112
 - 2.2.3 Capacitor under Sinusoidal Steady State / 113
 - 2.2.4 Brief Complex Number Theory Facts / 115
- 2.3 Time Domain Equations: Frequency Domain Impedance and Phasors / 123
 - 2.3.1 Phasors / 123
 - 2.3.2 The Impedance Concept / 124
 - 2.3.3 Purely Resistive Impedance / 126
 - 2.3.4 Inductive Impedance: Inductive Reactance / 127
 - 2.3.5 Purely Capacitive Impedance: Capacitive Reactance / 131
 - 2.3.6 R, L, and C Impedances Combinations / 133
- 2.4 Power in AC Circuits / 136
 - 2.4.1 AC Instantaneous Power Drawn by a Resistor / 137
 - 2.4.2 AC Instantaneous Power Drawn by a Capacitor / 137
 - 2.4.3 AC Instantaneous Power Drawn by an Inductor / 139
- 2.5 Dependent Voltage and Current Sources / 145
 - 2.5.1 Voltage-Controlled Voltage Source (VCVS) / 145
 - 2.5.2 Current-Controlled Voltage Source (CCVS) / 146
 - 2.5.3 Voltage-Controlled Current Source (VCCS) / 147
 - 2.5.4 Current-Controlled Current Source (CCCS) / 148
- 2.6 Summary of Key Points / 149
- Further Reading / 149
- Problems / 150

3	Circuit Theorems and Methods of Circuit Analysis	155
3.1	Introduction / 155	
3.2	The Superposition Method / 156	
3.2.1	Circuits Superposition / 160	
3.3	The Thévenin Method / 165	
3.3.1	Application of the Thévenin Method / 167	
3.4	Norton's Method / 172	
3.4.1	Source Transformations / 174	
3.4.2	Finding the Norton Equivalent Circuit Directly from the Given Circuit / 175	
3.5	The Mesh Method of Analysis / 179	
3.5.1	Establishing Mesh Equations. Circuits with Voltage Sources / 180	
3.5.2	Establishing Mesh Equations by Inspection of the Circuit / 186	
3.5.3	Establishing Mesh Equations When There Are also Current Sources / 189	
3.5.4	Establishing Mesh Equations When There Are also Dependent Sources / 196	
3.6	The Nodal Method of Analysis / 199	
3.6.1	Establishing Nodal Equations: Circuits with Independent Current Sources / 199	
3.6.2	Establishing Nodal Equations by Inspection: Circuits with Current Sources / 201	
3.6.3	Establishing Nodal Equations When There Are also Voltage Sources / 205	
3.6.4	Establishing Nodal Equations When There Are Dependent Sources / 207	
3.7	Which One Is the Best Method? / 210	
3.7.1	Superposition Theorem Highlights / 210	
3.7.2	Thévenin Theorem Highlights / 211	
3.7.3	Norton's Theorem Highlights / 211	
3.7.4	Source Transformations Highlights / 212	
3.7.5	Mesh Method of Analysis Highlights / 212	
3.7.6	Nodal Method of Analysis Highlights / 212	
3.8	Using all the Methods / 213	
3.8.1	Solving Using Superposition / 213	
3.8.2	Example 3.21: Solving the Circuit of Figure 3.36 by Thévenin / 216	
3.8.3	Example 3.22: Solving the Circuit of Figure 3.36 by Norton / 219	
3.8.4	Example 3.23: Solving the Circuit of Figure 3.36 Using Source Transformations / 221	

- 3.8.5 Example 3.24: Solving the Circuit of Figure 3.36 Using the Mesh Method / 223
- 3.8.6 Example 3.25: Solving the Circuit of Figure 3.36 Using the Nodal Method / 224
- 3.9 Summary and Conclusions / 225
- Further Reading / 225
- Problems / 226

4 First- and Second-Order Circuits under Sinusoidal and Step Excitations

233

- 4.1 Introduction / 233
- 4.2 The First-Order *RC* Low-Pass Filter (LPF) / 235
 - 4.2.1 Frequency Domain Analysis / 235
 - 4.2.2 Brief Introduction to Gain and the Decibel (dB) / 236
 - 4.2.3 *RC* LPF Magnitude and Phase Bode Plots / 238
 - 4.2.4 *RC* LPF Drawing a Bode Plot Using Just the Asymptotes / 241
 - 4.2.5 Interpretation of the *RC* LPF Bode Plots in the Time Domain / 244
 - 4.2.6 Why Do We Call This Circuit a LPF? / 245
 - 4.2.7 Time Domain Analysis of the *RC* LPF / 245
 - 4.2.8 First-order *RC* LPF under Pulse and Square-Wave Excitation / 248
 - 4.2.9 The *RC* LPF as an Integrator / 251
- 4.3 The First-Order *RC* High-Pass Filter (HPF) / 252
 - 4.3.1 *RC* HPF Frequency Domain Analysis / 253
 - 4.3.2 Drawing an *RC* HPF Bode Plot Using Just the Asymptotes / 254
 - 4.3.3 Interpretation of the *RC* HPF Bode Plots in the Time Domain / 257
 - 4.3.4 Why Do We Call This Circuit an HPF? / 258
 - 4.3.5 Time Domain Analysis of the *RC* HPF / 258
 - 4.3.6 First-Order *RC* LPF under Pulse and Square-Wave Excitation / 260
 - 4.3.7 The *RC* HPF as a Differentiator / 263
- 4.4 Second-Order Circuits / 265
- 4.5 Series RLC Second-Order Circuit / 266
- 4.6 Second-Order Circuit in Sinusoidal Steady State: Bode Plots / 275
- 4.7 Drawing the Second-Order Bode Plots Using Asymptotic Approximations / 278
- 4.8 Summary / 279
- Further Reading / 279
- Problems / 280

5	The Operational Amplifier as a Circuit Element	287
5.1	Introduction to the Operational Amplifier /	287
5.2	Ideal and Real Op Amps /	288
5.3	Brief Definition of Linear Amplifiers /	290
5.4	Linear Applications of Op Amps /	294
5.4.1	The Inverting Amplifier /	294
5.4.2	The Noninverting Amplifier /	306
5.4.3	The Buffer or Noninverting Amplifier of Unity Gain /	309
5.4.4	The Inverting Adder /	314
5.4.5	The Difference Amplifier /	316
5.4.6	The Inverting Integrator /	321
5.4.7	The Inverting Differentiator /	322
5.4.8	A Practical Integrator and Differentiator Circuit /	326
5.5	Op Amps Nonlinear Applications /	331
5.5.1	The Open-Loop Comparator /	332
5.5.2	Positive and Negative Voltage-Level Detectors Using Comparators /	332
5.5.3	Comparator with Positive Feedback (Hysteresis) /	336
5.6	Operational Amplifiers Nonidealities /	341
5.7	Op Amp Selection Criteria /	343
5.8	Summary /	347
	Further Reading /	348
	Problems /	348
	Appendix to Chapter 5 /	353
6	Electronic Devices: Diodes, BJTs, and MOSFETs	354
6.1	Introduction to Electronic Devices /	354
6.2	The Ideal Diode /	355
6.2.1	The Half-Wave Rectifier /	357
6.2.2	The Full-Wave Bridge Rectifier /	360
6.2.3	The Real Silicon Diode I - V Characteristics: Forward-Bias, Reverse-Bias, and Breakdown Regions /	363
6.2.4	Two More Realistic Diode Models /	367
6.2.5	Photodiode /	369
6.2.6	Light Emitting Diode (LED) /	369
6.2.7	Schottky-Barrier Diode /	371
6.2.8	Another Diode Application: Limiting and Clamping Diodes /	371
6.2.9	Diode Selection /	372
6.3	Bipolar Junction Transistors (BJT) /	374
6.3.1	Basic Concepts on Intrinsic, n -type and p -type Silicon Materials /	374
6.3.2	The BJT as a Circuit Element /	376

- 6.3.3 Bipolar Transistor *I-V* Characteristics / 377
- 6.3.4 Biasing Techniques of Bipolar Transistors / 382
- 6.3.5 Very Simple Biasing / 385
- 6.3.6 Resistor Divider Biasing / 387
- 6.3.7 Emitter Degeneration Resistor Biasing / 391
- 6.3.8 Self-Biased Staged / 394
- 6.3.9 Biasing Techniques of PNP Bipolar Transistors / 396
- 6.3.10 Small Signal Model and Single-Stage Bipolar Amplifier Configurations / 397
- 6.3.11 Common Emitter (C_E) Configuration / 399
- 6.3.12 Common Emitter (C_E) Configuration with Emitter Degeneration / 404
- 6.3.13 Common-Base (CB) Configuration / 407
- 6.3.14 The Common-Collector (CC) Configuration / 415
- 6.4 Metal Oxide Field Effect Transistor (MOSFET) / 420
 - 6.4.1 MOSFET *I-V* Characteristics / 424
 - 6.4.2 MOSFET Small Signal Model / 427
 - 6.4.3 MOSFET Biasing Techniques / 428
 - 6.4.4 Common Source (CS) Configuration / 434
 - 6.4.5 Common Source (CS) Configuration with Degeneration / 436
 - 6.4.6 Common Gate (CG) Configuration / 437
 - 6.4.7 Common Drain (CD) Configuration or Source Follower / 439
 - 6.4.8 Other MOSFETs: Enhancement Mode *p*-Channel and Depletion Mode (*n*-Channel and *p*-Channel) / 439
- 6.5 Summary / 443
- Further Reading / 446
- Problems / 446

7 Combinational Circuits

- 7.1 Introduction to Digital Circuits / 456
- 7.2 Binary Numbers: a Quick Introduction / 456
- 7.3 Boolean Algebra / 460
 - 7.3.1 *AND* Logic Operation 460
 - 7.3.2 *OR* Logic Operation (Also Called *Inclusive OR*, or *XNOR*) / 461
 - 7.3.3 *NOT* Logic Operation or Inversion—*NAND* and *NOR* / 462
 - 7.3.4 Exclusive *OR* Logic Operation or *XOR* / 463
 - 7.3.5 DeMorgan’s Laws, Rules, and Theorems / 464
 - 7.3.6 Other Boolean Algebra Postulates and Theorems / 465
 - 7.3.7 The Duality Principle / 466
 - 7.3.8 Venn Diagrams / 467

- 7.4 Minterms: Standard or Canonical Sum of Products (SOP) Form / 467
- 7.5 Maxterms: Standard or Canonical Product of Sums (POS) Form / 472
- 7.6 Karnaugh Maps and Design Examples / 473
 - 7.6.1 Two-Variable Karnaugh Maps / 474
 - 7.6.2 Three-Variable Karnaugh Maps / 479
 - 7.6.3 Four-Variable Karnaugh Maps / 484
 - 7.6.4 Five-Variable Karnaugh Maps / 487
- 7.7 Product of Sums Simplifications / 490
- 7.8 Don't Care Conditions / 491
- 7.9 Logic Gates: Electrical and Timing Characteristics / 495
 - 7.9.1 Gates Key Electrical Characteristics / 497
 - 7.9.2 Gates Key Timing Characteristics / 499
- 7.10 Summary / 500
- Further Reading / 500
- Problems / 500

8 Digital Design Building Blocks and More Advanced Combinational Circuits

503

- 8.1 Combinational Circuits with More than One Output / 503
- 8.2 Decoders and Encoders / 510
 - 8.2.1 Making Larger Decoders with Smaller Ones / 515
 - 8.2.2 Encoders / 517
- 8.3 Multiplexers and Demultiplexers (MUXes and DEMUXes) / 519
 - 8.3.1 Multiplexers / 521
 - 8.3.2 Building Larger Multiplexers / 522
 - 8.3.3 De-Multiplexers / 526
- 8.4 Signed and Unsigned Binary Numbers / 527
 - 8.4.1 One's Complement Representation of Binary Numbers: Addition / 527
 - 8.4.2 Two's Complement Representation of Binary Numbers: Addition / 531
 - 8.4.3 Other Numbering Systems / 533
- 8.5 Arithmetic Circuits: Half-Adders (HA) and Full-Adders (FA) / 533
 - 8.5.1 Building Larger Adders with Full-Adders / 536
 - 8.5.2 Notes about Full-Adder Timing / 540
 - 8.5.3 Subtracting with a 4-bit Adder Using 1's Complement Representation / 540
 - 8.5.4 Subtracting with a 4-bit Adder Using 2's Complement Representation / 542

- 8.6 Carry Look Ahead (CLA) or Fast Carry Generation / 543
- 8.7 Some Short-Hand Notation for Large Logic Blocks / 546
- 8.8 Summary / 547
- Further Reading / 548
- Problems 548

9 Sequential Logic and State Machines 550

- 9.1 Introduction / 550
- 9.2 Latches and Flip-Flops (FF) / 552
 - 9.2.1 *NAND*-Implemented \bar{R}/\bar{S} Latch / 557
 - 9.2.2 *SR-Latch* with Enable / 559
 - 9.2.3 Master/Slave *SR*-Flip-Flop / 561
 - 9.2.4 Master/Slave *JK* Flip-Flop / 565
 - 9.2.5 Master/Slave *T* and *D* Type Flip-Flops / 568
- 9.3 Timing Characteristics of Sequential Elements / 571
 - 9.3.1 Timing of Flip-Flops with Additional Set and Reset Control Inputs / 571
- 9.4 Simple State Machines / 574
 - 9.4.1 *SR* Flip-Flop Excitation Table / 578
 - 9.4.2 *T* Flip-Flop Excitation Table / 580
 - 9.4.3 *D* Flip-Flop Excitation Table / 581
- 9.5 Synchronous State Machines General Considerations / 592
 - 9.5.1 Synchronous State Machine Design Guidelines / 592
 - 9.5.2 Timing Considerations: Long and Short Path Analyses / 595
- 9.6 Summary / 599
- Further Reading / 600
- Problems / 600

10 A Simple CPU Design 603

- 10.1 Our Simple CPU Instruction Set / 603
- 10.2 Instruction Set Details: Register Transfer Language (RTL) / 605
- 10.3 Building a Simple CPU: A Bottom-Up Approach / 607
 - 10.3.1 The Registers / 607
 - 10.3.2 The Memory Access Path or Memory Interface / 610
 - 10.3.3 The Arithmetic and Logic Unit (ALU) / 611
 - 10.3.4 The Program Counter (PC) / 611
- 10.4 Data Path Architecture: Putting the Logic Blocks Together / 615
 - 10.4.1 Data Path: *LDA* Instruction Fetch, Decode and Execution RTL / 615
 - 10.4.2 All Other Instructions: Fetch, Decode and Execution: RTL / 618

10.5	The Simple CPU Controller /	620
10.5.1	State Assignments and Controller Implementation /	622
10.6	CPU Timing Requirements /	626
10.7	Other System Pieces: Clock, Reset and Power Decoupling /	628
10.7.1	Clock /	628
10.7.2	Reset /	628
10.7.3	Power Decoupling /	631
10.8	Summary /	633
	Further Reading /	633
	Problems /	633

PREFACE

For several years I taught an introductory analog and digital essentials course for the University of California Extensions at Berkeley and Santa Cruz. Teaching there motivated me to put together, under one cover, a textbook that contains fundamentals of electrical, electronics, analog, and digital circuits. That is the reason for the word “essentials” in the title. There are not that many books in the market that try to accomplish this task in about 600 pages.

The book is divided into 10 chapters. It is useful for surveys of electrical and electronics courses, for college students as well as practicing scientists and engineers; it is also useful for introductory circuit courses at the undergraduate level. The book provides many examples from beginning to end. Within the examples, specific components part numbers were avoided to prevent this book from becoming obsolete. The book can be used by students who have some to no previous knowledge of the material, and for graduate-level and working professionals’ circuit courses. The prerequisites for using this book are freshman-level calculus and algebra. Nevertheless, the level of math needed is quite light. The book is a gentle introduction to electrical and electronic circuit analysis with many examples.

Physical concepts are emphasized not only with text but also with specially prepared figures that should help the first-time readers study the material.

This book emphasizes problem solving, using different circuit analysis methodologies. These techniques allow readers to understand when one method is more appropriate than another. Ultimately, it is the student who is responsible for adopting the methods that make the most sense. No one thinks exactly in the same way. An example is differentiation and integration. For some people, differentiation is simpler than integration; for others, is the other way around.

Chapter 1 covers the three basic circuit elements: resistors, inductors, and capacitors. Additionally, *ideal* and *real* independent DC current and voltage sources are addressed. Chapter 2 emphasizes AC circuits, as they are applied to the three basic circuit elements. Their *time-domain* and *frequency-domain* behavior is seen throughout examples. A brief refresher on *operations with complex numbers* is embedded in this chapter and not in an appendix for reasons of reading continuity. The concept of power drawn by a circuit and its different types are addressed. The chapter ends with the coverage of dependent

voltage and current sources. Chapter 3 addresses methods to solve circuits; it should be studied with the greatest attention and as many problems with different circuit analysis methods as possible should be solved. From a practical point of view, this is a core chapter to master.

Chapter 4 describes with plenty of detail the behavior of first-order and second-order circuits in the time and frequency domains. Many textbooks do not put as much emphasis on first-order circuits, because they are considered too simple. It has been my experience with students that first-order high-pass filters are particularly more difficult to understand than first-order low-pass filters. Chapter 5 is dedicated to *operational amplifiers*. Even though op amps consist of to-be-covered electronic components, it is useful to have the reader think with some high level of abstraction. Under some conditions op amps are seen as functional blocks and not as circuits with transistors and resistors. Linear and nonlinear applications with op amps are covered with many examples.

Chapter 6 covers electronic devices. Much information on devices is provided. One can say that entire books have been written just on the electronic components addressed by this chapter. The textbook takes a systematic approach to study the circuits using diodes and transistors, hardly dwelling on device physics. Chapter 7 begins with digital logic. *Combinational* (and not “combinatorial,” as it is sometimes mistakenly called) logic circuits do not have any memory. Logic operations or Boolean algebra is presented, and logic simplification methods such as the Karnaugh map method are illustrated. Chapter 8 deals with more advanced combinational circuits such as multiplexers, decoders, and some arithmetic circuits. A method to produce a very fast arithmetic sum of two operands is covered. Chapter 9 is about state machine design or sequential logic. Sequential logic has memory, unlike combinational logic, and it is the core subject when designing logic circuits that perform useful and complete functions. Chapter 10 describes piece by piece the construction of a simple CPU. The CPU basic functional blocks, such as its instruction set, the data path architecture, its memory interface, and the control logic, are described step by step. Some insights into capacitor power decoupling and reliable reset circuits are also presented. The problems at the end of this chapter provide tremendous insight into the CPU functionality. This chapter can be thought as a very light introduction to a computer architecture course.

Writing this book has been a very rewarding experience for me. This book should be very useful to college students and those professionals who need an essential analog and digital source.

I want to thank my wife Ruty and daughter Denise for their infinite patience and support while I was preparing the manuscript.

Eduardo (Ed) M. Lipiansky

ABOUT THE AUTHOR

Eduardo (Ed) Lipiansky received his undergraduate degree in electrical engineering from the National University of La Plata, Argentina (UNLP). He performed graduate studies at the University of California, Berkeley, obtaining a master of science degree in electrical engineering. Mr. Lipiansky has 25 years of industry experience, having worked at Varian Associates, Tandem Computer, Sun Microsystems, Cisco Systems, and Google.

He is author or co-author of six patents; four have been issued by the U.S. Patent Office, and two more have been submitted. Mr. Lipiansky's key interests are maintenance and diagnostics subsystems for servers, networking line cards, analog and digital electronic design for medical instrumentation and computers, and power engineering. Ed wrote *Embedded Systems Hardware for Software Engineers* (2011), which deals with more advanced hardware concepts and can be used as an add-on to the present textbook. For about 20 years, he taught a variety of courses such as circuit analysis, digital design, operational amplifiers, and microprocessor interfacing techniques at the University of California Berkeley and Santa Cruz Extensions. Mr. Lipiansky lives with his family in the San Francisco Bay area in northern California.